

LONG ANSWER QUESTIONS:

1. Draw and explain the components of a Digital Computer.

A computer is a machine that can perform computation. A computation involves the following three components:

- **Input:** The user gives a set of input data.
- **Processing:** The input data is processed by a well-defined and finite sequence of steps.
- **Output:** Some data available from the processing step are output to the user.

A *digital computer* accepts, processes and outputs data in digitized forms (as opposed to analog forms).

The basic components of a digital computer

In order that a digital computer can solve problems, it should be equipped with the following components:

- **Input devices**

These are the devices using which the user provides input instances. In a programmable computer, input devices are also used to input programs. Examples: keyboard, mouse.

- **Output devices**

These devices notify the user about the outputs of a computation. Example: screen, printer.

- **Processing unit**

The central processing unit (CPU) is the brain of the computing device and performs the basic processing steps. A CPU typically consists of:

- **An arithmetic and logical unit (ALU):** This provides the basic operational units of the CPU. It is made up of units (like adders, multipliers) that perform arithmetic operations on integers and real numbers, and of units that perform logical operations (logical and bitwise AND, OR etc.).
- **A control unit:** This unit is responsible for controlling flow of data and instructions.
- **General purpose registers:** A CPU usually consists of a finite number of memory cells that work as scratch locations for storing intermediate results and values.

- **External memory**


The amount of memory (registers) resident in the CPU is typically very small and is inadequate to accommodate programs and data even of small sizes.

Out-of-the-processor memory provides the desired storage space. External memory is classified into two categories:

- **Main (or primary) memory:** This is a high-speed memory that stays close to the CPU. Programs are first loaded in the main memory and then executed. Usually main memory is volatile, i.e., its contents are lost after power-down.
- **Secondary memory:** This is relatively inexpensive, bigger and low-speed memory. It is normally meant for off-line storage, i.e., storage of programs and data for future processing. One requires secondary storage to be permanent, i.e., its contents should last even after shut-down. Examples of secondary storage include floppy disks, hard disks and CDROM disks.

- **Buses**

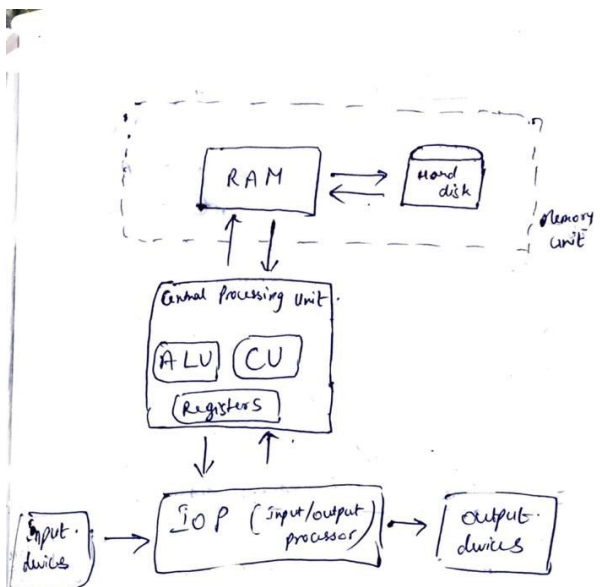A bus is a set of wires that connect the above components. Buses are responsible for movement of data from input devices, to output devices and from/to CPU and memory.



Digital computer

3 main components

1. CPU

- ALU

- CU

- Registers (store data temporarily)

2. RAM

3. IOP

2. Discuss about the principle of Von Neumann Architecture.

ANS) Historically there have been 2 types of Computers:

1. **Fixed Program Computers** – Their function is very specific and they couldn't be programmed, e.g. Calculators.
2. **Stored Program Computers** – These can be programmed to carry out many different tasks, applications are stored on them, hence the name.

The modern computers are based on a stored-program concept introduced by John Von Neumann. In this stored-program concept, programs and data are stored in a separate storage unit called memories and are treated the same. This novel idea meant that a computer built with this architecture would be much easier to reprogram.


von Neumann architecture

The **von Neumann architecture** describes a general framework, or structure, that a computer's hardware, programming, and data should follow. Although other structures for computing have been devised and implemented, the vast majority of computers in use today operate according to the von Neumann architecture.


von Neumann envisioned the structure of a computer system as being composed of the following components:

 1. **ALU:** The **Arithmetic-Logic unit** that performs the computer's computational and logical functions. e.g. Addition, Subtraction, Comparisons. It performs Logical Operations, Bit Shifting Operations, and Arithmetic Operation.
2. **RAM:** Memory; more specifically, the computer's main, or fast, memory, also known as **Random Access Memory(RAM)**.
3. **Control Unit:** This is a component that directs other components of the computer to perform certain actions, such as directing the fetching of data or instructions from memory to be processed by the ALU; and
4. **Input/Output Devices** – Program or data is read into main memory from the *input device* or secondary storage under the control of CPU input instruction.


Output devices are used to output the information from a computer. If some results are evaluated by computer and it is stored in the computer, then with the help of output devices, we can present it to the user.



 
An example of computer architecture base on the von Neumann architecture is the desktop **personal computer**.



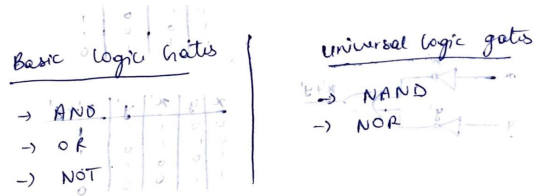NAND REALIZATION (DERIVING OTHER GATES USING NAND):



 
Realisation of ~~AND~~ NOT gate using NAND



$$\begin{aligned} x \cdot y &= (x \cdot y)' \\ &= (x \cdot x)' \\ &= x' \end{aligned}$$


Realisation of AND using NAND

$$x \cdot y = ((x \cdot y)')'$$

 




Realisation of OR using NAND

$$x + y = ((x + y)')' = (x' \cdot y')'$$

 

NOR REALIZATION(DERIVING OTHER GATES USING NOR):

NOR REALIZATION

   

3. List the Boolean Identities. (Or) State the laws of Boolean algebra.

1.	Law of Identity	$A = A$ $\overline{\overline{A}} = A$
2.	Commutative Law	$A \cdot B = B \cdot A$ $A + B = B + A$
3.	Associative Law	$A \cdot (B \cdot C) = A \cdot B \cdot C$ $A + (B + C) = A + B + C$
4.	Idempotent Law	$A \cdot A = A$ $A + A = A$
5.	Double Negative Law	$\overline{\overline{A}} = A$
6.	Complementary Law	$A \cdot \overline{A} = 0$ $A + \overline{A} = 1$
7.	Law of Intersection	$A \cdot 1 = A$ $A \cdot 0 = 0$
8.	Law of Union	$A + 1 = 1$ $A + 0 = A$
9.	DeMorgan's Theorem	$\overline{AB} = \overline{A} + \overline{B}$ $\overline{A + B} = \overline{A} \cdot \overline{B}$
10.	Distributive Law	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ $A + (BC) = (A + B) \cdot (A + C)$
11.	Law of Absorption	$A \cdot (A + B) = A$ $A + (AB) = A$
12.	Law of Common Identities	$A \cdot (\overline{A} + B) = AB$ $A + (\overline{A}B) = A + B$

(13. $X + X'Y = X + Y$)

4. Simplify the following Boolean Expression using Boolean Identities and draw the logic diagram for the simplified expression.

a. $A + BC' + ABD' + ABCD$

b. $A'BC + AC$

c. $A'B + ABC' + ABC$

d. $(BC' + A'D)(AB' + CD')$

$$\Rightarrow A + BC' + ABD' + ABCD$$

$$\Rightarrow A + B(C' + AD' + ACD)$$

$$\Rightarrow A + B(C' + A(D' + CD)) \quad [x + x'y = x + y]$$

$$\Rightarrow A + B(C' + A(D' + C))$$

$$\Rightarrow A + B(C' + AD' + AC) \quad [x + x'y = x + y]$$

$$\Rightarrow A + B(C' + A + AD')$$

$$\Rightarrow A + B(C' + A(1 + D')) \quad [1 + A = 1]$$

$$\Rightarrow A + B(C' + A)$$


$$\Rightarrow AC' + A + BC' + AB$$

$$\Rightarrow A(1 + C') + BC' + AB \quad [1 + A = 1]$$

$$\Rightarrow A + BC' + AB$$

$$\Rightarrow A(1 + B) + BC' \quad [1 + A = 1]$$

$$\Rightarrow A + BC'$$

 


$$(b) A'BC + AC$$

$$[x + x'y = x + y]$$

$$\Rightarrow C(A'B + A)$$

$$\Rightarrow C(A + B)$$

$$\Rightarrow AC + BC$$

 

$$(c) A'B + ABC' + ABC$$

$$\Rightarrow B(A' + AC' + AC)$$

$$\Rightarrow B(A' + A(C' + C)) \quad [A + \bar{A} = 1]$$

$$\Rightarrow B(A + A') \quad [A + \bar{A} = 1]$$

$$\Rightarrow B$$

$$\underline{B}$$

$$(d) (BC' + A'D)(AB' + CD')$$

$$\Rightarrow ABB'C' + BCC'D' + AA'B'D + A'CDD'$$

$$\Rightarrow 0 + 0 + 0 + 0$$

$$\Rightarrow 0$$

5. Write the rules for simplifying the given Boolean expression into Sum-of-Products (SoP) form using K-Maps.

6. Write the rules for simplifying the given Boolean expression into Product-of-Sums (PoS) form using K-Maps.

K-MAPS:

Karnaugh Map (K-map) :-

The K-map is a graphical representation that provides a systematic method for simplifying the Boolean Expression.

Two Variable K-map :-

For n variable K-map 2^n cells are required.

Therefore for 2-variable K-map, $2^2 = 4$ cells will be required.

A \ B	0	1
0	00	01
1	10	11

A \ B	\bar{B}	B
\bar{A}	$\bar{A}\bar{B}$	$\bar{A}B$
A	$A\bar{B}$	AB

A \ B	0	1
0	0	1
1	2	3

Rules followed for K-map simplification -

1. Groups do not include any cell containing a zero

A \ B	0	1
0	0	0
1	0	0

X

A \ B	0	1
0	0	1
1	1	1

✓

2. Groups may be horizontal or vertical, but not diagonal.

A \ B	0	1
0	0	1
1	1	0

X

A \ B	0	1
0	1	1
1	1	1

✓

3. Groups must contain 1, 2, 4, 8 or 2^n cells.

A \ BC	00	01	11	10
0	1	1	1	1
1				1

X

A \ BC	00	01	11	10
0	1	1	1	1
1				1

✓

4. Each group should be as large as possible.

A \ BC	00	01	11	10
0	1	1	1	1
1				1

X

(This simplification does not give minimum literals)

A \ BC	00	01	11	10
0	1	1	1	1
1				1

✓

SUM OF PRODUCTS:

Grouping of cells for simplification -

→ Adjacent cells which have 1's can be grouped ^{together} in 2^n power

$2^1 = 2$ adjacent cell can be grouped (Pair)

$2^2 = 4$ " " " " (Quad)

$2^3 = 8$ " " " " (Octet)

$2^4 = 16$ " " " "

AB \ CD	CD	CD	CD	CD
AB	1			
AB				
AB				
AB				
AB				

$$(\bar{A}\bar{B} + \bar{A}B) \cdot \bar{C}\bar{D} = \bar{A}(\bar{B} + B) \cdot \bar{C}\bar{D} = \bar{A}\bar{C}\bar{D}$$

$$\bar{A}(\bar{B} + B) \cdot \bar{C}\bar{D} = \bar{A}\bar{C}\bar{D}$$

$$\bar{A}\bar{C}\bar{D}$$

$$F = \bar{A}\bar{C}\bar{D} + BCD + A\bar{B}\bar{D}$$

AB \ CD	CD	CD	CD	CD
AB	1			
AB				
AB				
AB				
AB				

$$F = BD + \bar{B}\bar{D}$$

AB \ CD	CD	CD	CD	CD
AB	1			
AB				
AB				
AB				
AB				

$$F = C + \bar{D}$$

PRODUCT OF SUMS:

Q. Simplify $F(ABC) = \bar{A}BC + B\bar{C} + AB\bar{C} + A\bar{B}C$ using K-map. in SOP form and POS form.

SOP Simplification:

$F = \sum m(2, 3, 5, 6)$
 $F = \prod M(0, 1, 4, 7)$

$F = B\bar{C} + \bar{A}B + A\bar{B}C$

Pos Simplification:

$\bar{F} = \bar{B}\bar{C} + \bar{A}\bar{B} + ABC$
 $F = \overline{\bar{B}\bar{C} + \bar{A}\bar{B} + ABC}$
 $F = (B+C) \cdot (A+B) \cdot (\bar{A} + \bar{B} + \bar{C})$

(OR)

$F = (B+C) \cdot (A+B) \cdot (\bar{A} + \bar{B} + \bar{C})$

Q. Simplify $F(ABCD) = \prod M(0, 1, 3, 6, 7, 8, 9, 11, 13, 14, 15)$

Pos:

$\bar{F} = BC + AD + CD + \bar{B}\bar{C}$
 $F = \overline{BC + AD + CD + \bar{B}\bar{C}}$
 $F = (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{D}) \cdot (\bar{C} + \bar{D}) \cdot (B + C)$

DON'T CARE CONDITION:

Don't care is represented as x. It can be grouped with either 0 (POS) or 1 (SOP). It is not necessary to use it, only use it if the group becomes bigger.

2. Minimize with the help of K-map GGETU-2012-13.

$F(A,B,C,D) = \sum m(1,3,4,6,8,9,11,13,15) + \sum d(0,2,4)$

sol

AB \ CD	00	01	11	10
00	X	1	1	X
01	1			1
11		1	1	X
10	1	1	1	0

$F = AD + \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{D}$

7. Simplify the following function into Sum-of-Products form and draw the corresponding Logic Diagram.

a. $f(A, B, C, D) = \sum (0, 2, 8, 9, 10, 11, 12, 14, 15)$

b. $f(w, x, y, z) = \sum (2, 3, 4, 5, 6, 7, 11, 14, 15)$

(7)

(a) $f(A, B, C, D) = \sum (0, 2, 8, 9, 10, 11, 12, 14, 15)$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1			1
$\bar{A}B$				
$A\bar{B}$				
AB				

$\Rightarrow AC + A\bar{B} + A\bar{D} + B\bar{D}$

(b) $f(w, x, y, z) = \sum (2, 3, 4, 5, 6, 7, 11, 14, 15)$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{x}$				
$\bar{w}x$				
$w\bar{x}$				
wx				


$\Rightarrow \bar{w}y + yz + wx + \bar{w}x$

8. Simplify the following function into Product-of-Sums form and draw the corresponding Logic Diagram.

a. $f(A, B, C, D) = \sum (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$


b. $f(w, x, y, z) = \sum (0, 1, 2, 4, 5, 7, 11, 15)$

 a) $f(A, B, C, D) = \sum (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$



$\Rightarrow (A + \bar{B} + D) \cdot (B + \bar{D})$

 b) $f(w, x, y, z) = \sum (0, 1, 2, 4, 5, 7, 11, 15)$



$\Rightarrow (\bar{w} + y) \cdot (w + z) \cdot (\bar{x} + \bar{y} + z)$
 $(w + x + y + \bar{z})$

9. Simplify the following function into Sum-of-Products form and Product-of-Sums form using Don't-Care Conditions.

$$f(w, x, y, z) = \sum (0, 1, 2, 3, 7, 8, 10)$$

$$d(w, x, y, z) = \sum (5, 6, 11, 15)$$

$f(w, x, y, z) = \sum (0, 1, 2, 3, 7, 8, 10)$
 $d(w, x, y, z) = \sum (5, 6, 11, 15)$

wx \ yz	00	01	11	10
00	1	1	1	1
01		X	1	X
11			X	
10	1		X	1

→ 3 maps

$$(x'z') + (w'x') + (w'z)$$

wx \ yz	00	01	11	10
00				
01	0	X		X
11	0	0	X	0
10		0	X	

$$(w' + x') \cdot (w' + z') \cdot (x' + y)$$

10. Write the procedure for designing a combinational circuit.

combinational circuits

The inter connection of various logic gates to achieve certain functionality.

Features of combinational Circuits

combinational circuits take ' m ' no. of inputs & ' n ' no. of outputs

- 2) The output doesn't depend upon the previous state of the circuit
- 3) They don't have memory & the circuits can have one or multiple outputs.



Analysis

Analysis of a combination circuit involves deriving a ^{simplified} boolean expression from the given logic diagram.

Design


Design is the process of expressing the given task in the form of a logic diagram.

Design Process for a combinational ckt

- 1) Analyse the ^{understand} problem statement
- 2) Take the required no. of variables & name them.
- 3) Draw the truth table by taking these variables as input & represent the outputs depending on the task or functionality.
- 4) Simplify the truth table using either k-maps or boolean laws

11. Design the combinational circuit for

 a. Half-Adder - The Half-Adder is a combinational circuit of adding two numbers as two inputs and produce out two outputs. The adder is used to perform OR operation of two single bit binary numbers. The x and y bits are two input states, and 'carry' cout and 'sum' s are two output states of the half adder.



Design a Half-adder ckt.


x & y } inputs

Sum & Carry } outputs.


x	y	Σ	Count
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = xy' + x'y = x \oplus y$$

x	y	Σ
0	0	0
0	1	1
1	0	1
1	1	0

 

 b. Full-Adder - The half adder is used to add only two numbers. To overcome this problem, the full adder was developed. The full adder is used to add three 1-bit binary numbers x , y , and carry C_{in} . The full adder has three input states and two output states i.e., sum s and carry out.



Full adder

$2^3 - 1$


x, y, C_{in} { i/p }

s, C_{out} { o/p }

x	y	C_{in}	s	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$x \backslash y C_{in}$	00	01	11	10
0		0		1
1	1		1	

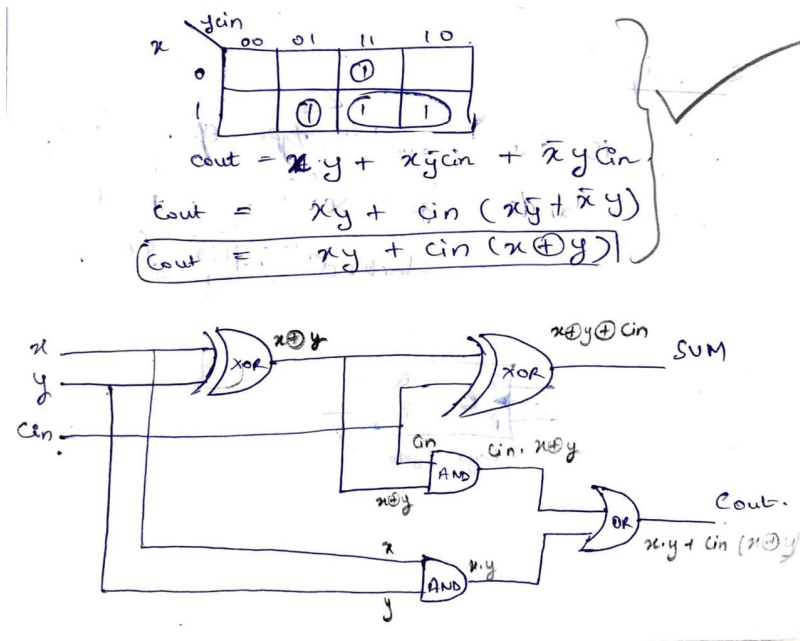$s = \underline{x \oplus y \oplus C_{in}}$



12. Explain the operation of the following flip-flops.

Flip-Flops:-

- Flip-flop is a memory element which is capable of storing one bit of information and it is used in clocked sequential circuits.
- A Flip-flop has two outputs, one for normal value and other for complement value of the bit stored in it.
- A flip-flop can maintain a binary state indefinitely (as long as power is delivered to the circuit) until directed by an input signal to switch states.
- A flip-flop is also known as bistable multivibrator.

 


Fig. Block diagram of a flip-flop

- Flip-flops are of different types depending on how their inputs and clock pulses cause transition between two states.
- There are four basic types: SR, JK, D and T flip-flops.



Flip Flops

- A flip flop is a binary cell capable of storing one (1) bit of info.
- It has 2 o/p's, one for normal value & other for complement.
- A clock signal directs the change of state of flip-flop.
- SR flip flop
- D flip-flop
- JK flip-flop
- T flip-flop.

  a. SR-Flip-flop

SR flip-flop

- * It is the simplest type of flip flop.
- * It stands for set reset flip flop.
- * It is a clocked flip flop.



Truth table / characteristics

I/P			O/P
S	R	Q_n (Present state)	Q_{n+1} (Next state)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Indeterminate
1	1	1	Indeterminate

→ If $S=0$ & $R=0$,
the next state of SR flip-flop is
same as present state.

→ If $S=0$ & $R=1$, the next state
will be 0.

→ If $S=1$ & $R=0$, next state will
be 1.

→ when both $S=R=1$, the next
state will be indeterminate.



Reduced truth table / characteristic table

I/P			O/P	Remarks
S	R	Q_n	Q_{n+1}	States & conditions
0	0	X	Q_n	Hold state condition $S=R=0$
0	1	X	0	Reset state condition $S=0, R=1$
1	0	X	1	Set state condition $S=1, R=0$
1	1	X	Indeterminate	Indeterminate state condition $S=R=1$

  b. JK- Flip-flop

JK flip-flop

- Refine & improved version of SR flip flop.
- Introduced to solve the problem of indeterminate state in SR flip flop where both $S = R = 1$.



I/P			O/P
J	K	Σn	ΣnH
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

- when $J=K=0$, the next state is same as present state of the flip-flop.
- when $J=0$ & $K=1$, the next state is 0.
- when $J=1$ & $K=0$, $Q_{n+1} = 1$
- when $J=K=1$, $Q_{n+1} = \overline{Q_n}$


I/P			O/P	Remark
J	K	Q_n	Q_{n+1}	States & conditions
0	0	X	Q_n	Hold state condition $J=K=0$
0	1	X	0	Reset state condition $J=0, K=1$
1	0	X	1	Set state condition $J=1, K=0$
1	1	X	Q_n'	


c. D- Flip-flop

D flip-flop

- D (data) flip flop -
- A slight modification of SR flip flop
- Inserting an inverter b/w S & R

D	$Q(t+1)$	
0	0	Clear to 0
1	1	Set to 1

 

 

S	R
1	0
0	1

It is same as SR flip flop, except,
S & R are connected by not gate.

Truth Table:-

Clk	D	Q_{n+1}
0	x	Q_n
1	0	0
1	1	1

Char. Table:-


Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

$$Q_{n+1} = D$$

 d. T-Flip-flop

T flip-flop :-

The T flip-flop is a single input version of JK flip-flop as shown in figure.




Fig(a) Logic diagram

Characteristic Table


Q(t)	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

T	Q(t+1)
0	Q(t)
1	Q-bar(t)

 

Fig(b) Graphic symbol

T-Flip-flop

 

I/P	O/P	
	Present state	Next state
T	Q _n	Q _{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

13. Draw and explain the excitation tables of the following flip-flops.

e. SR-Flip-flop

f. JK- Flip-flop


g. T- Flip-flop

h. D- Flip-flop

SR Flip-flop				D Flip-flop		
Q(t)	Q(t+1)	S	R	Q(t)	Q(t+1)	D
0	0	0	X	0	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	0
1	1	X	0	1	1	1

JK flip-flop				T flip-flop		
Q(t)	Q(t+1)	J	K	Q(t)	Q(t+1)	T
0	0	0	x	0	0	0
0	1	1	x	0	1	1
1	0	x	1	1	0	1
1	1	x	0	1	1	0


ENCODER:

 

Encoding: converting more no. of bits to less no. of bits.

Decoding: The lesser no. of bits received have to be converted to equivalent no. of original bits.

Encoder

 

has 4 i/p's y_0, y_1, y_2, y_3
& 2 o/p's A_0, A_1

(arrows should exactly touch the block)

An encoder is a combinational circuit which has 2^n inputs & n outputs
(as it is inverted commens)

Depending on which i/p is ~~active~~ ^{active} high, the output represents the equivalent binary value.

I/Ps				O/Ps	
Y_3	Y_2	Y_1	Y_0	A_1	A_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1

High.

(for $Y_0 = 0 \therefore 00$ binary of 0)



$Y_1 = 1 \therefore 01$ " " 1

$Y_2 = 2 \therefore 10$ " " 2

$Y_3 = 3 \therefore 11$ " " 3

$$A_1 = Y_2 + Y_3$$

$$A_0 = Y_1 + Y_3$$

  

y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0	a_2	a_1	a_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	1	1	1	1

DRAWBACKS OF ENCODER:

Drawbacks of encoder.


- (If none of the inputs are high, i.e. all are zeroes)
- When all outputs are zeroes, there is an ambiguity with encoder whether the 0^{th} i/p is active high or all the i/p are zeroes
 - If more than one i/p is active high, the encoder doesn't represent the proper output. To overcome this drawback there is another type of encoder known as priority encoder which allows assigning priorities to the i/p's.
 - If both Y_6 & Y_7 are active high, the o/p is going to be 110 when Y_6 is given higher priority.

combination ckt → uses logic gates
sequential ckt → flip flops

DECODER:

Decoder.

 - It is a combinational ckt. that performs the reverse operation of encoder.
- It has 'n' input lines & max. of '2ⁿ' output lines.
- One of these outputs will be active high based on the combination of inputs present, when the decoder is enabled.



Enable E	I/P S		Outputs			
	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

$$Y_0 = E A_1' A_0'$$

$$Y_1 = E A_1' A_0$$

$$Y_2 = E A_1 A_0'$$

$$Y_3 = E A_1 A_0$$


→ For decoder if there are n inputs, max no. of outputs are 2^n .

$$Y_0 = E A_1' A_0'$$


$$Y_1 = E A_1' A_0$$

$$Y_2 = E A_0' A_1$$

$$Y_3 = E A_1 A_0$$

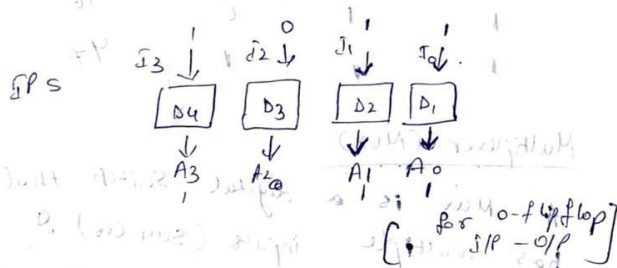

construction of octal to binary decoder.

 

$A_2 = E$	A_1	A_0	O/P
0	0	0	Y_0
0	0	1	Y_1
0	1	0	Y_2
0	1	1	Y_3
1	0	0	Y_4
1	0	1	Y_5
1	1	0	Y_6
1	1	1	Y_7

MULTIPLEXER:

Multiplexer (Mux)

A Mux is a digital switch that has multiple inputs (sources) & a single output (destination).


The select lines determine which input is connected to the output.

→ Mux types.

2 to 1 (1 select line)
4 to 1 (2 " ")
8 to 1 (3 " ")
16 to 1 (4 " ")


→ It is a combinational circuit that has max. of 2^n data inputs, 'n' selection lines & single o/p line.

4x1 multiplexer.

 

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

8x1 Multiplexer

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

